

**International Islamic University Islamabad Faculty of
Engineering and Technology Department of
Electrical and Computer Engineering**

VLSI DESIGN LAB



EXPERIMENT Lab 7: Sequential Logic: Hierarchical Design of Half and Full Adders in LT-Spice

Name of Student: Bushra Nazir Ahmed

Roll No.: 1071-F22

Date of Experiment: 20-Nov-2025


Lab Performance Report#7

[CLO1, 2, 3]


- **Task#1:** Create the schematic of **1-Bit half adder** using XOR and AND gate symbols. Perform its transient analysis to verify the truth table. Write your observations about the output waveforms
- **Task#2:** “Save as” and modify the circuit of 1-Bit Half adder and generate its symbol. Use this symbol to create a **1-Bit Full Adder** circuit. Perform its transient analysis to verify the truth table. Write your observations about the output waveforms
- **Task#3:** “Save as” and modify the circuit of 1-Bit Full adder and generate its symbol. Use this symbol to create a **2-Bit Full Adder** circuit. Perform its transient analysis to verify the truth table. Write your observations about the output waveforms.
- Submit a report in MS-Word format in Google Class whose structure should be:
 - Title Page
 - Screenshots of each of the above tasks. **Each task** should be arranged on **one page** i.e. schematic on top, its waveform/outputs below it and your remarks/analysis in a few lines.
- **Caution:** There is no unique solution to this assignment. All submissions should be different, like wiring of your schematic and selection of circuit parameters, inputs and outputs. **Zero marks will be awarded for exact copies, so avoid sharing your assignments with friends.**

Task 1 :

schematic

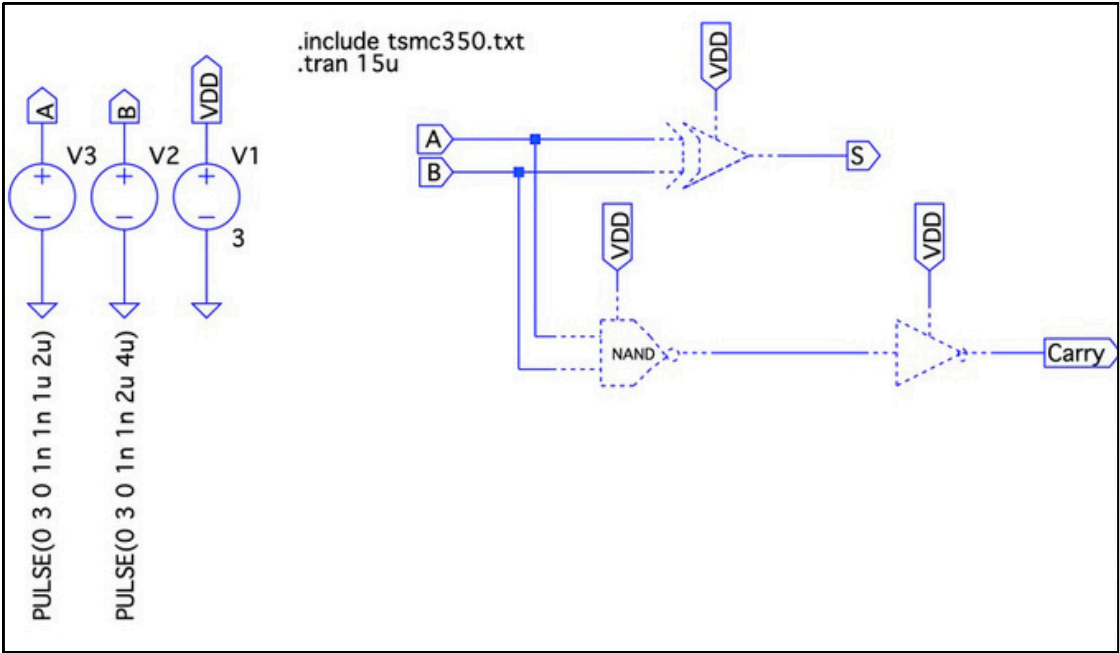


WAVEFORM

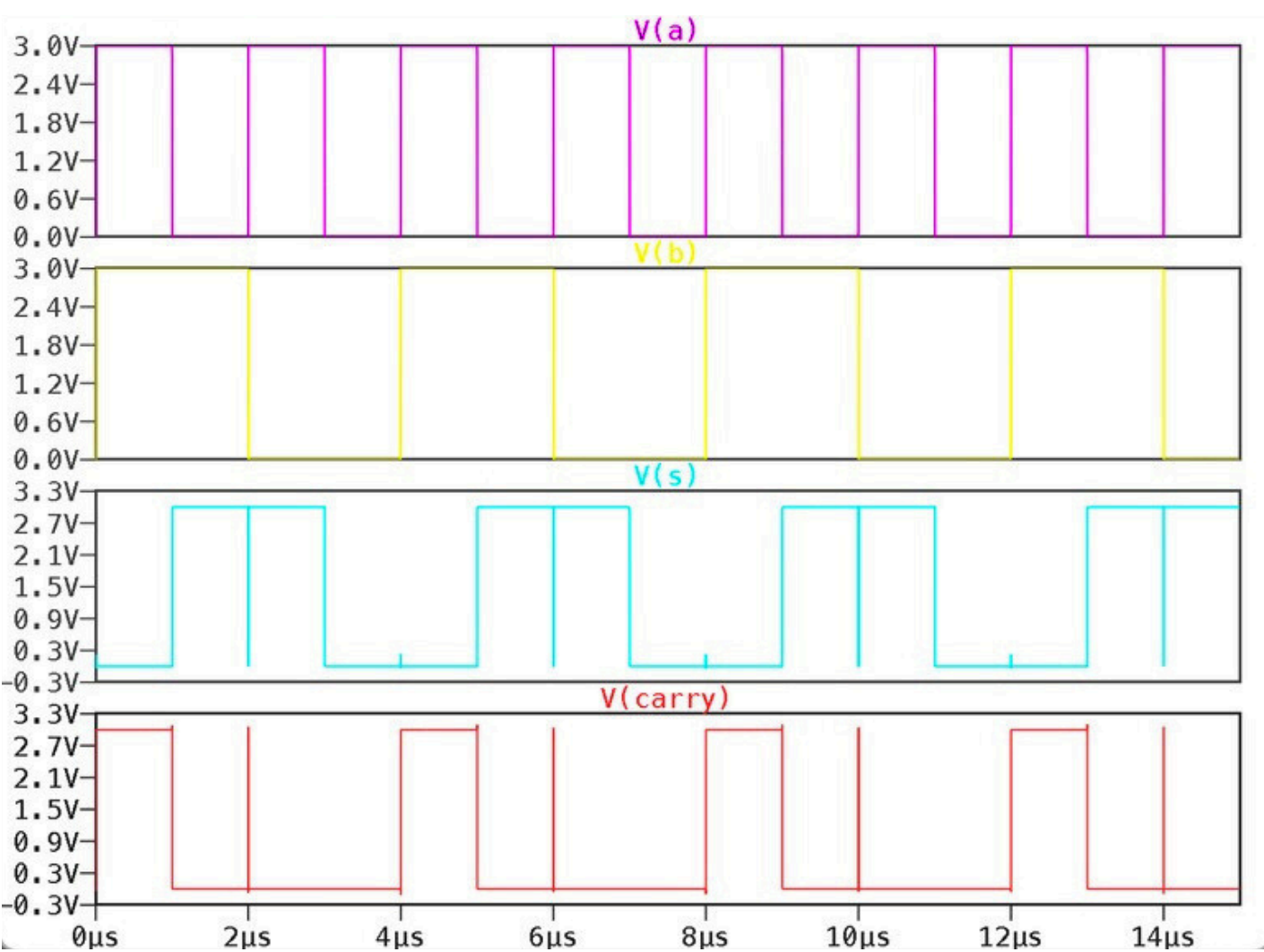


Task2 :

schematic

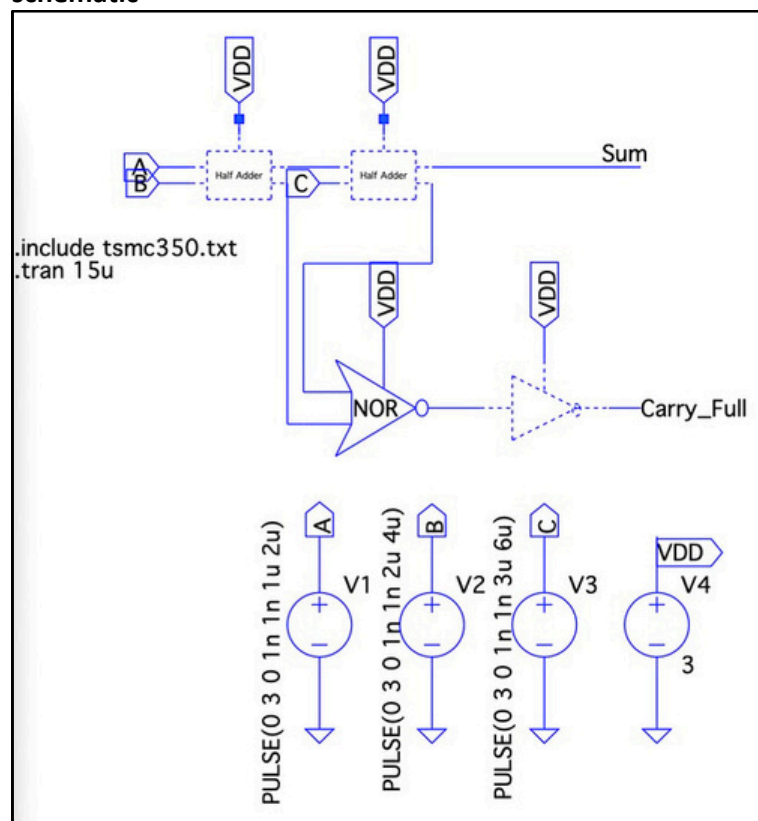**truthTable**


Input			Output	
A	B	C	Sum = S	Carry = C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

WAVEFORM

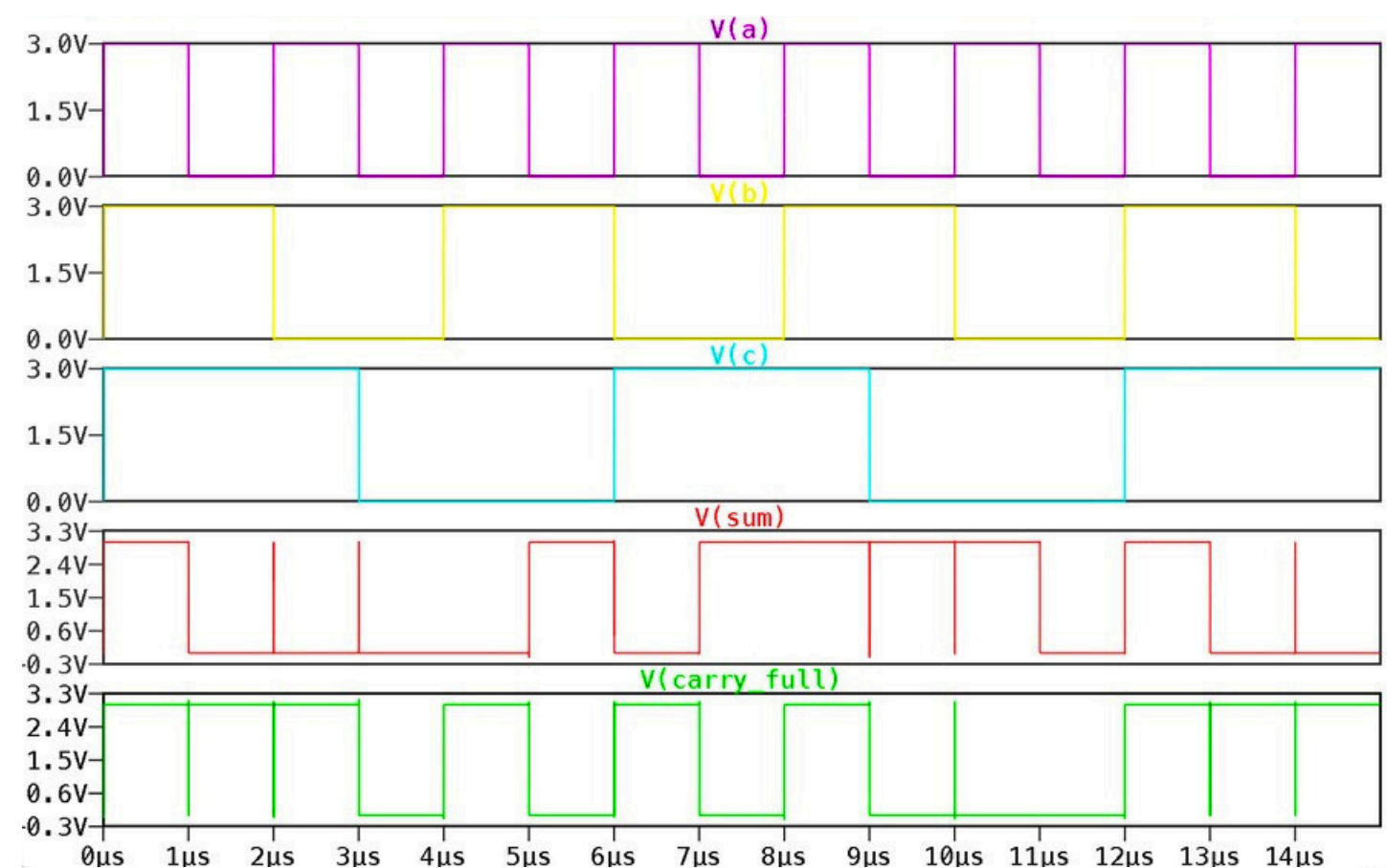

task 3 :

schematic

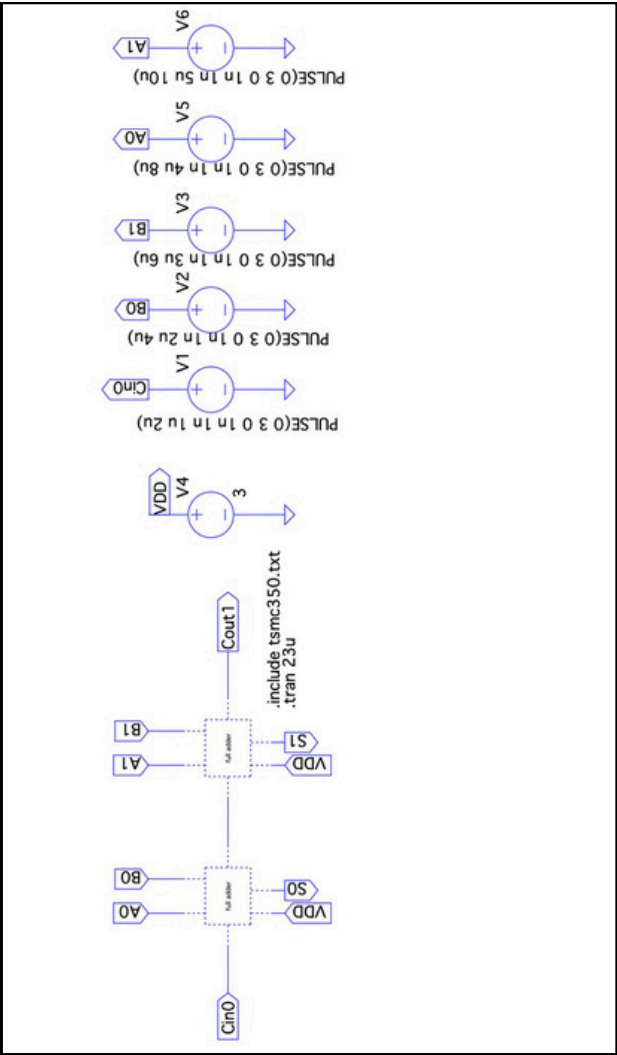

truthTable

A ₁ A ₀	B ₁ B ₀	C ₀	S1	S0	Cout1	Cout0
00	00	0	0	0	0	1
00	00	1	0	1	0	1
00	01	0	0	1	0	1
01	00	0	0	1	0	1
00	01	1	1	0	0	1
01	00	1	1	0	0	1
01	01	0	1	0	0	1
01	01	1	1	1	0	1
00	10	0	1	0	0	1
00	10	1	1	1	0	1
00	11	0	1	1	0	1
01	10	0	1	1	0	1
00	11	1	0	0	1	0
01	10	1	0	0	1	0
01	11	0	0	0	1	0
01	11	1	0	1	1	0
10	00	0	1	0	0	1
10	00	1	1	1	0	1
10	01	0	1	1	0	1
11	00	0	1	1	0	1
10	01	1	0	0	1	0
11	00	1	0	0	1	0
11	01	0	0	0	1	0
11	01	1	0	1	1	0
10	10	0	0	0	1	0
10	10	1	0	1	1	0
10	11	0	0	1	1	0
10	11	1	1	0	1	0
11	10	0	0	1	1	0
11	10	1	1	0	1	0
11	11	0	1	0	1	0
11	11	1	1	1	1	0

WAVEFORM

