

**International Islamic University Islamabad Faculty of  
Engineering and Technology Department of  
Electrical and Computer Engineering**

**VLSI DESIGN LAB**



**EXPERIMENT # 04: XOR and XNOR Gate Design and optimization using  
LTSpice**


**Name of Student:** Bushra Nazir Ahmed

**Roll No.:** 1071-F22

**Date of Experiment:** 9-oct-2025

# Lab Performance Report#4

 - **Task#1:** Design an XNOR Gate as in Figure below for a load capacitance of 1pF and  $V_{DD}=3.3V$ . Select **Pulse A** and **Pulse B** inputs of your own choice ( $T > 500ns$  for both inputs; make sure that each of  $t_r$  and  $t_f$  should be 5ns.). Both inputs should be dissimilar.
- [Perform following analysis for XNOR Gate](#)
- **Analysis#1:** Perform the transient analysis of your schematic for **3 Time Periods duration** of Pulse A or B; i.e. whichever has larger time period. Vary the PMOS and NMOS transistor sizes till you get a symmetric output waveform. (Note: symmetric means  $t_{plh} = t_{phl}$ )
- **Analysis#2:** Analyze and find Average Propagation Delay through waveforms. Calculate the propagation delay via **“.meas”** commands. Compare both results for  **$t_{plh}$** ,  **$t_{phl}$**  and  **$t_p$**
- **Analysis#3:** Analyze and find **Average Power** drawn from  $V_{DD}$  through waveform. Now calculate the same via **“.meas”** command as well. Give your remarks about the power dissipation of this circuit.



- Submit a report in both **“Printed Form”** within class and **“MS-Word format”** in Google Class whose structure should be:
  - Title Page
  - Screenshot of above tasks and analysis i.e. schematic, waveforms and analysis. Each task should be arranged as schematic on top, and then its waveform below it.
- **Instructions:** There is no unique solution to this assignment. All submissions should be different like wiring of your schematic and selection of pulse waveform and other parameters”. **Zero marks will be awarded for exact copies, so avoid sharing your assignments with friends.**

## Analysis 1, 2, 3:


### Netlist

```
* /Users/bushra/Desktop/LTspice/XNOR.asc
M1 N002 A_bar VDD VDD PMOS l=350n w=90u
M2 XNOR B_bar N002 VDD PMOS l=350n w=90u
M3 N001 A VDD VDD PMOS l=350n w=90u
M4 XNOR B N001 VDD PMOS l=350n w=90u
M5 XNOR A_bar N003 0 NMOS l=350n w=10u
M6 N003 B 0 0 NMOS l=350n w=10u
M7 XNOR A N004 0 NMOS l=350n w=10u
M8 N004 B_bar 0 0 NMOS l=350n w=10u
VDD VDD 0 3.3
VA A 0 PULSE(0 3.3 0 5n 5n 270n 540n)
VB B 0 PULSE(0 3.3 0 5n 5n 255n 510n)
XX1 A VDD A_bar symb
XX2 B VDD B_bar symb
C1 XNOR 0 1p

* block symbol definitions
.subckt symb Vin VDD Vout
M1 VDD Vin Vout N001 PMOS l=350n w=2.5u
M2 Vout Vin 0 N002 NMOS l=350n w=1u
.include tsmc350.txt
.ends symb

.model NMOS NMOS
.model PMOS PMOS
.lib /Users/bushra/Library/Application Support/LTspice/lib/cmp/
standard.mos
.include tsmc350.txt
.tran 1620n
.meas tran tphi_B1 TRIG v(B) V(VDD)/2 FALL=1 TARG v(XNOR) V(VDD)/2
FALL=1
.meas tran tphi_B2 TRIG v(B) V(VDD)/2 RISE=1 TARG v(XNOR) V(VDD)/2
FALL=1
.meas tran tphi_A1 TRIG v(A) V(VDD)/2 FALL=1 TARG v(XNOR) V(VDD)/2
RISE=1
.meas tran tphi_A2 TRIG v(A) V(VDD)/2 RISE=1 TARG v(XNOR) V(VDD)/2
RISE=1
.meas tran tphi param max(tphi_B1, tphi_B2)
.meas tran tphi param max(tphi_A1, tphi_A2)
.meas P_D PARAM (tphi+tphi)/2
.meas TRAN Avg-P AVG -V(VDD)*I(VDD) FROM=0 TO=540n
.backanno
.end
```


### WAVEFORM

 

### SPICE Output Log

```
Search
tphi_b1=2.59282e-09 FROM 2.625e-07 TO 2.65093e-07
tphi_b2=2.62593e-07 FROM 2.5e-09 TO 2.65093e-07
tphi_a1=3.54835e-11 FROM 2.775e-07 TO 2.77535e-07
tphi_a2=2.75035e-07 FROM 2.5e-09 TO 2.77535e-07
tphi: max(tphi_b1, tphi_b2)=2.62593e-07
tphi: max(tphi_a1, tphi_a2)=2.75035e-07
p_d: (tphi+tphi)/2=2.68814e-07
avg-p: AVG(-v(vdd)*i(vdd))=6.94571e-05 FROM 0 TO 5.4e-07
Total elapsed time: 0.102 seconds
```

### schematic

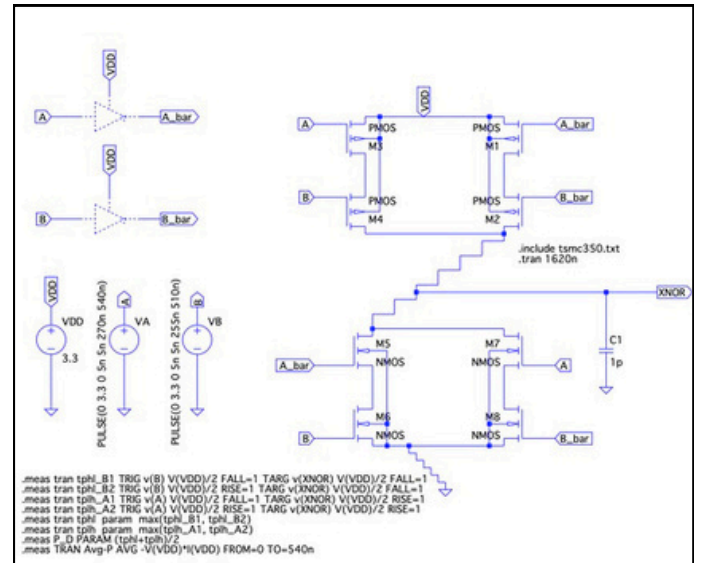

## observations:

### Analysis #1 – Transient Analysis:

Successfully performed transient analysis for 3 time

periods and adjusted transistor sizes. Output

waveform is now symmetric ( $t_{plh} \approx t_{phl}$ ).

### Analysis #2 – Propagation Delay:

Correctly measured  $t_{plh}$  and  $t_{phl}$  using .meas commands. The calculated average delay ( $t_p \approx 268.8$  ns) matches the waveform results closely.

### Analysis #3 – Power Analysis:

Accurately measured average power using waveform and .meas command. The circuit shows reasonable power dissipation ( $\approx 69.5 \mu\text{W}$ ).