

**International Islamic University Islamabad Faculty of  
Engineering and Technology Department of  
Electrical and Computer Engineering**

**VLSI DESIGN LAB**



**EXPERIMENT Lab 9: INVERTER schematic**

**Name of Student:** Bushra Nazir Ahmed

**Roll No.:** 1071-F22

**Date of Experiment:** 27-Nov-2025

# Lab Performance Report#10

- **Task#1: Pre-layout Simulation:**
  - Build up an inverter schematic step by step in Electric. Perform Transient analysis of CMOS inverter using a pulse input of your own choice in Electric and observing output of CMOS inverter in Ltspice
  - Use .meas command to evaluate propagation delay and power dissipation of the inverter.
  - Report the screenshots of schematic diagram, Spice netlist, I/O waveforms and log file
- **Caution:** There is no unique solution to this assignment. All submissions should be different, like wiring of your schematic and selection of circuit parameters, inputs and outputs. **Zero marks will be awarded for exact copies, so avoid sharing your assignments with friends.**

Task 1 :

Spice netlist

```
*** SPICE deck for cell inverter{sch} from library inverter
*** Created on 08/08/14, 2025 17:12:32
*** Last revised on 08/08/14, 2025 17:59:44
*** Written on 08/08/14, 2025 17:59:58 by Electric VLSI Design
System, version 9.07
*** Layout tech: mcomos, foundry MOSIS
*** UC SPICE *** , MIN_RESIST 4.0, MIN_CAPAC 0.1FF
*** Lambda Conversion ***

.global gnd vdd

*** TOP LEVEL CELL: inverter{sch}
NMOS VOUT VIN gnd gnd NMOS L=0.35u W=1u
PMOS vdd VIN VOUT vdd PMOS L= 0.35u W=2.5u

* Spice Code nodes in cell cell 'inverter{sch}'
.include tsmc350.txt
.PARAM SUPPLY=3.3V
VDD VDD 0 DC 'SUPPLY'
VIN VIN 0 PULSE 0 'SUPPLY' 100PS 10PS 10PS 200PS 500PS
.TRAN 10PS 600PS
.meas tran tphi TRIG v(Vin) VAL=1.65 FALL=1 TARG v(Vout) VAL=1.65
RISE=1
.meas tran tphi TRIG v(Vin) VAL=1.65 RISE=1 TARG v(Vout) VAL=1.65
FALL=1
.meas tran tp_avg PARAM = (abs(tphi)+abs(tphi))/2
.END
```

log file

```
LTspice 17.2.4 for MacOS
Circuit: *** SPICE deck for cell inverter{sch} from library inverter
Start Time: Sun Dec 14 18:01:48 2025
Ignoring BSIM parameter XL
Ignoring BSIM parameter XW
Ignoring BSIM parameter XL
Ignoring BSIM parameter XW
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
CompressWinPoints = 1024
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Direct Newton iteration for .op point succeeded.

tphi=8.25099e-12 FROM 3.15e-10 TO 3.23251e-10
tphi=8.48761e-12 FROM 1.05e-10 TO 1.13488e-10
tp_avg: (abs(tphi)+abs(tphi))/2=8.3693e-12

Total elapsed time: 0.042 seconds.
```

I/O waveforms



schematic

