

**International Islamic University Islamabad Faculty of
Engineering and Technology Department of
Electrical and Computer Engineering**

VLSI DESIGN LAB



**EXPERIMENT Lab 9: Design and Performance Analysis of D Flip-Flop in
LT-Spice**

Name of Student: Bushra Nazir Ahmed

Roll No.: 1071-F22

Date of Experiment: 27-Nov-2025

Lab Performance report

- Lab Task:


1. Verify the working of **Edge Triggered D-latch** via timing diagrams of your circuit. Apply input combinations of your choice to evaluate performance completely.
2. Verify the working of **Master Slave D-Flipflop** via timing diagrams of your circuit. Apply input combinations of your choice to evaluate performance completely.

- Post Lab Task:


3. Make a **4-bit binary down counter** using **D-Flipflops**. Evaluate and correlate the output timing diagrams with the truth table.

Task 1 :

schematic

 


WAVEFORM

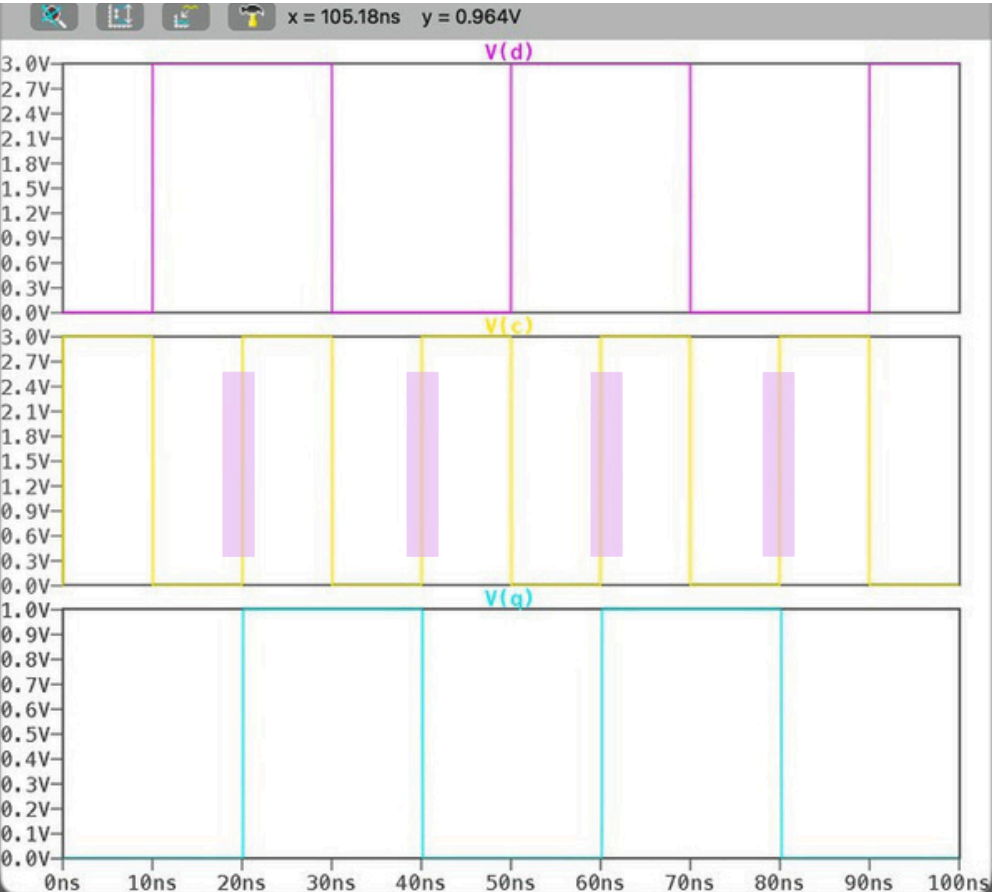


The edge-triggered D-latch operation was verified using timing diagrams. The output changes only at the clock edge.

Task 2 :

schematic

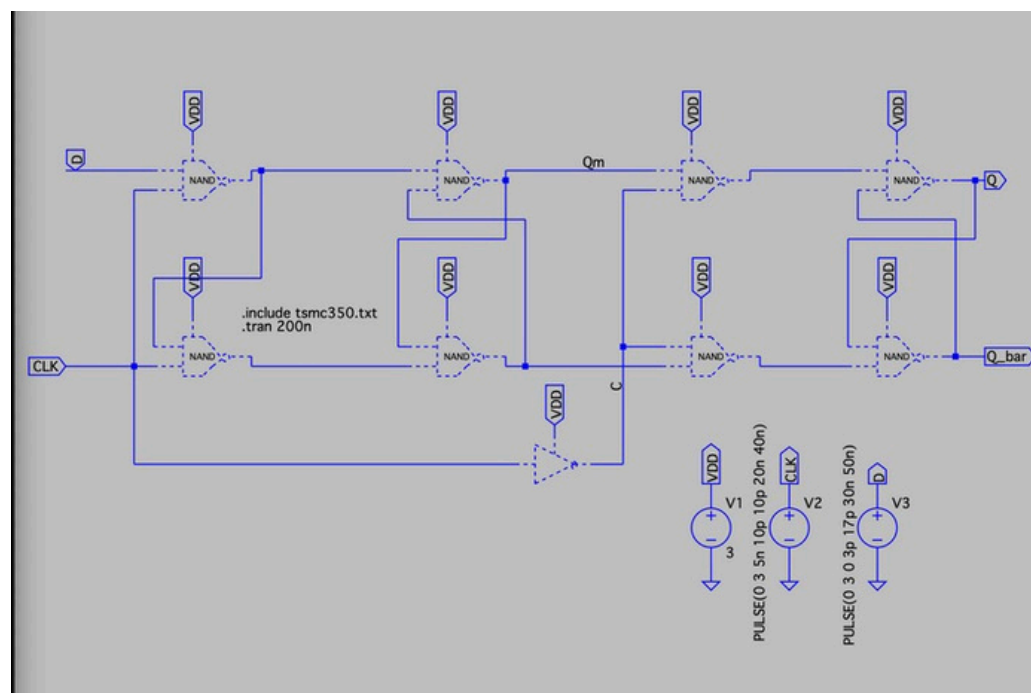


WAVEFORM

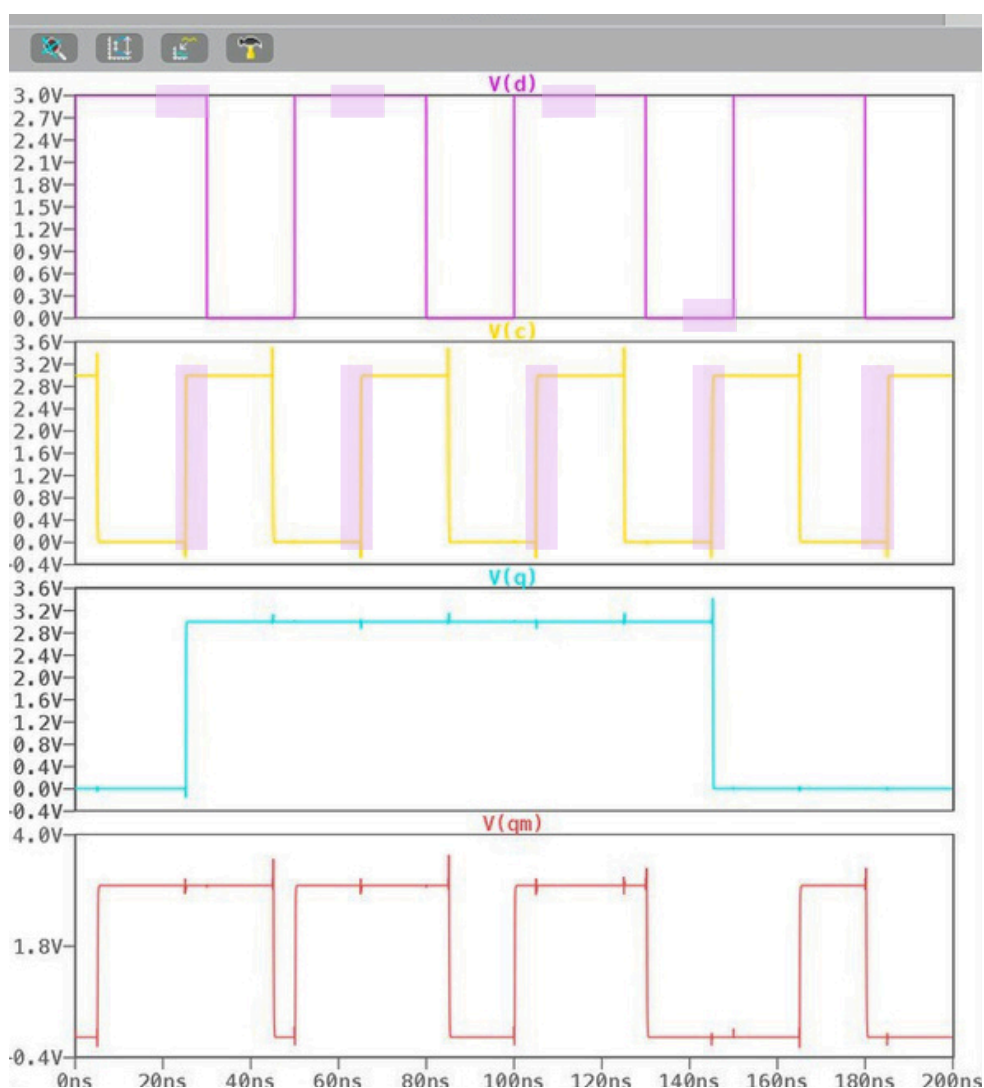

the working of the master-slave D flip-flop was verified through timing diagrams. The results show that the output updates only on the clock edge, eliminating race conditions and ensuring stable operation.


Task 3 :

schematic

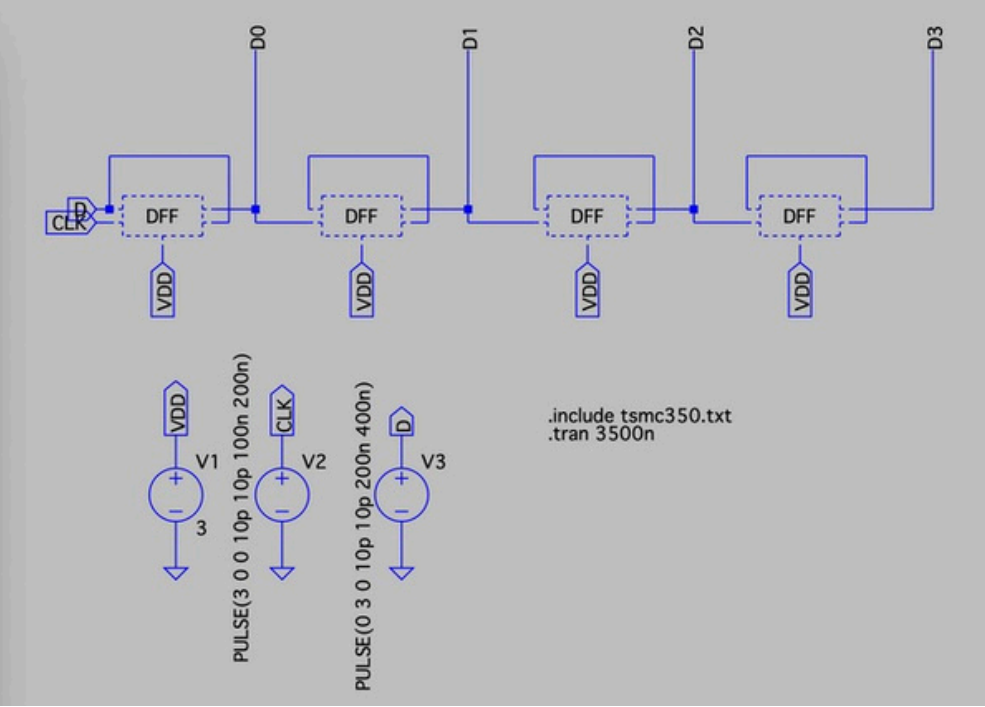

A 4-bit binary down counter was implemented using D flip-flops. The timing diagrams matched the truth table.

WAVEFORM

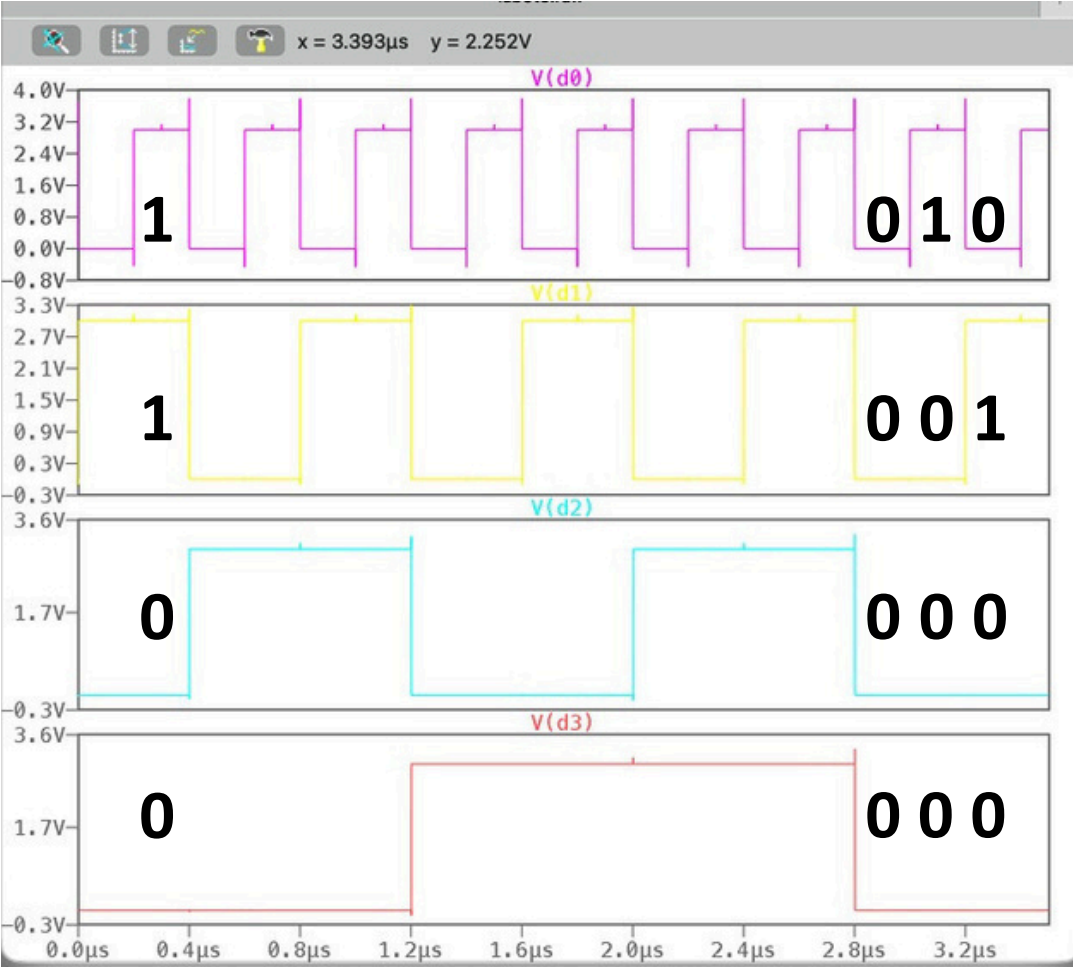

Count	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
0	0	0	0	0