

**International Islamic University Islamabad Faculty of  
Engineering and Technology Department of  
Electrical and Computer Engineering**

**VLSI DESIGN LAB**



**EXPERIMENT Lab 8:** Design and Performance Analysis of SRAM Cells  
in LT- Spice

**Name of Student:** Bushra Nazir Ahmed

**Roll No.:** 1071-F22

**Date of Experiment:** 20-Nov-2025

# Lab Performance Report#8

- **Task#1:** Create a schematic of 6-Transistor based SRAM cell that has logic 1 stored in the node connected with bit\_line. (Note: Use initial condition .ic V(Q)=VDD and .ic V(Q\_bar)=0 directives where Q and Q\_bar are the internal nodes of SRAM cell that are connected to Bit line and Bit\_Bar through access transistors). Simulate and record the resulting plots.
- **Task#2:** Using Word\_Line and write driver transistors flip the data stored at node Q and Q\_bar. Simulate and record the resulting plots.
- **Task#3:** Create a schematic of the SRAM Sense amplifier Pre\_charge the Bit and Bit\_Bar to VDD Now apply a voltage difference of 0.5 V between the bit and bit\_bar lines and sense it using Word\_Line and Sense\_En inputs. The outputs Data and Data\_Bar should establish a perfect logic 0 and logic 1. Simulate and record the resulting plots.


Submit a report in MS-Word format in Google Class whose structure should be:

- Title Page
- Screenshots of each of the above tasks. Each task should be arranged on one page i.e. schematic on top, its waveform/outputs below it and your remarks/analysis in a few lines.

Caution: There is no unique solution to this assignment. All submissions should be different, like wiring of your schematic and selection of circuit parameters, inputs and outputs. Zero marks will be awarded for exact copies, so avoid sharing your assignments with friends.

## Task 1 & 2 :

### schematic

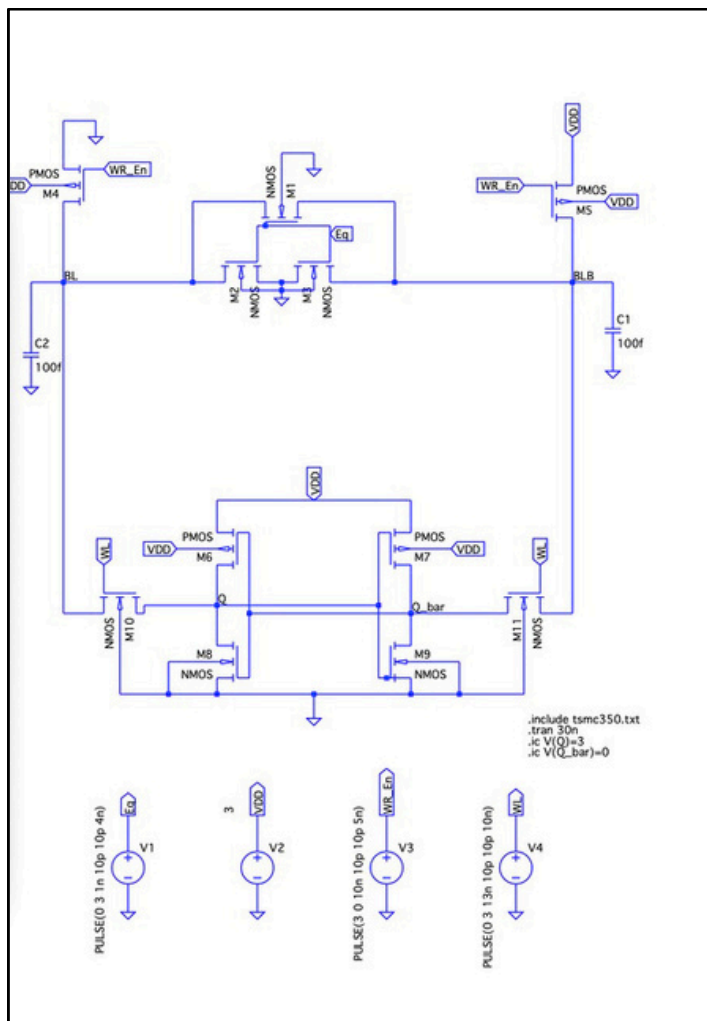

A 6T SRAM cell was designed and initialized to store logic


'1' at Q and logic '0' at Q using initial conditions.

The stored data was successfully flipped using the

Word\_Line and write drivers, as confirmed by the


simulation results.

### WAVEFORM

 

### Task 3 :

#### schematic

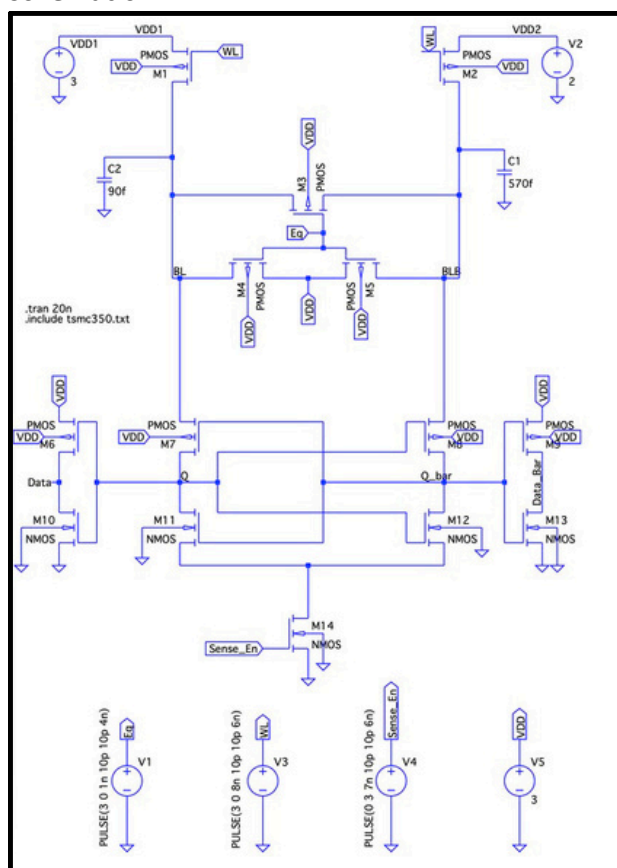

The SRAM sense amplifier was simulated by precharging Bit and Bit\_Bar to VDD and applying a 0.5 V differential voltage.

When Sense\_En was enabled, the amplifier correctly produced full logic levels at Data and Data\_Bar.

#### WAVEFORM

