

**International Islamic University Islamabad Faculty of  
Engineering and Technology Department of  
Electrical and Computer Engineering**

**VLSI DESIGN LAB**



**EXPERIMENT # 05: Design and Performance Analysis of the MOSFET Amplifiers**

**Name of Student:** Bushra Nazir Ahmed

**Roll No.:** 1071-F22

**Date of Experiment:** 5-Nov-2025

# Lab Performance Report#5

**Task#1 Creating Schematic:** Create a schematic of an NMOS biased in Voltage Divider (source bypassed) configuration. Choose transistor length and resistances values of your own whereas for NMOS,  $W = 10 \times L$ . You may consult any text or a reference book. Try to choose a unique circuit. **Task#2 Generating Symbol:** Create the symbol of the amplifier that you made in Task#1. The symbol should have four I/O pins i.e.  $V_{in}$ ,  $V_{out}$ ,  $V_{DD}$ , and  $V_{SS}$ .

**Task#3 DC Operating Point Analysis:** Create a new schematic using the same symbol created in Task#2 and connecting it to  $V_{DD} = 3.3\text{ V}$  and  $V_{SS} = \text{Gnd}$ . Perform DC operating point analysis. Take a screenshot of the output popup window. Write your remarks about the output values. See if the NMOS is biased in saturation mode or not. If it is not in saturation, then change the resistance values of task#1. Re-simulate and repeat the process till NMOS comes in saturation mode. Take screenshot of your adjusted circuit of task#1 along with the results of DC operating point analysis for making the report.

**Task#4 DC Sweep Analysis:** Create a new schematic using the same symbol created in Task#2 and connecting it to  $V_{DD} = 3.3\text{ V}$  and  $V_{SS} = \text{Gnd}$ . Perform DC Sweep Analysis analysis by varying input voltage from 0 to 3.3 volt in steps of 0.1V. Plot the output vs input voltage results. Take screenshot of the schematic output. Write your remarks about the output. Why the output varies with input voltage?

**Task#5 AC Transient Analysis:** “Save as” the final circuit of task#3 (.asc file) and create a new schematic from it. Insert coupling capacitors at input and output pins. Choose suitable values for coupling capacitors. Insert R at output node choosing suitable value. Select any sine wave signal

whose amplitude is between 5mV to 50mV and frequency value between 1k to 15k Hz. Perform the transient analysis of this circuit. Report the screenshots of the schematic, output voltage, current and power waveforms and gain of the amplifier calculated via spice .meas commands.


**Task#6 AC Sweep Analysis (Frequency Analysis):** “Save as” the final circuit of task#5 (.asc file) and create a new schematic from it. Perform AC Sweep Analysis by varying input voltage frequency from 1Hz to 1Meg Hz keeping amplitude fixed at 70 mV. Plot the output/input ratio results. Take screenshots of the schematic and output. Observe and report the cut-off frequency and type of frequency response (i.e., Low Pass, High Pass, or Band Pass etc).

o Submit the report in printed form whose structure should be:


- o Title Page
- o Screenshots of each of the above tasks. Each task should be arranged on one page i.e. schematic/spice\_netlist on top, its waveform/outputs below it and your remarks/analysis in a few lines.
- o Caution: There is no unique solution to this assignment. All submissions should be different, like wiring of your schematic and selection of circuit parameters, inputs and outputs. Zero marks will be awarded for exact copies, so avoid sharing your assignments with friends.

## Task 1, 2, 3 :

### schematic creation

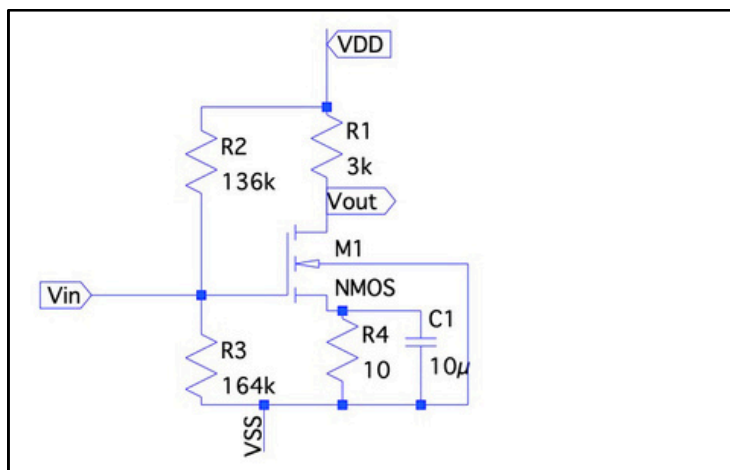

### schematic

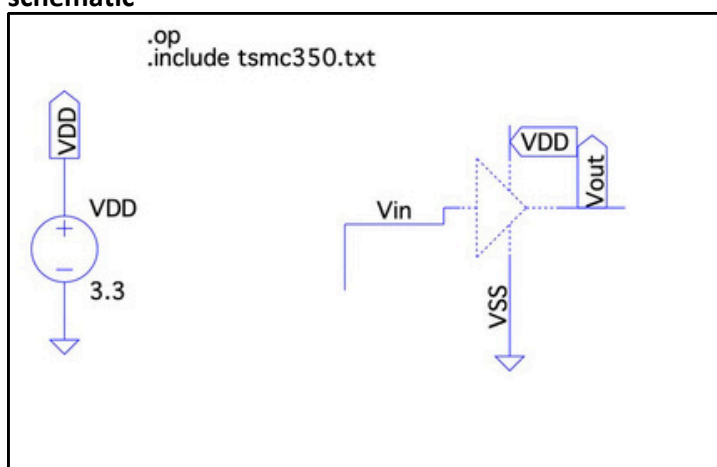

### SPICE Output Log

```
lab5tasks123.log
--- B5IM3 MOSFETS ---
Name:      m:x1:1
Model:     nmos
Id:        4.82e-04
Vgs:       1.80e+00
Vds:       1.85e+00
Vbs:       -4.82e-03
Vth:       7.64e-01
Vdsat:     5.38e-01
Gm:        6.36e-04
Gds:       4.49e-05
Gmb:       1.43e-04
Cbd:       0.00e+00
Cbs:       0.00e+00
Cgsbv:     8.96e-16
Cgdov:     8.96e-16
Cgbv:      3.03e-17
dQgdVgb:   5.35e-15
dQgdVdb:   -7.90e-16
dQgdVsb:   -4.29e-15
dQddVgb:   -2.32e-15
dQddVdb:   8.34e-16
dQddVsb:   1.91e-15
dQbdVgb:   -7.22e-16
dQbdVdb:   1.78e-17
dQbdVsb:   -4.31e-16

Operating Bias Point Solution:
V(vdd)           3.3      voltage
V(vout)          1.85443  voltage
V(vin)           1.804    voltage
I(Vdd)           -0.000492855 device_current
Ix(x1:VIN)       -3.38813e-21 subckt_current
Ix(x1:VDD)        0.000492855 subckt_current
Ix(x1:VSS)       -0.000492855 subckt_current
Ix(x1:VOUT)      -4.15298e-15 subckt_current



Total elapsed time: 0.135 seconds.
```

### observations:

The NMOS was found to operate in saturation region after adjusting the bias resistors, confirming correct biasing conditions as  $V_{DS} > V_{DS}(SAT)$

#### Task4 :

##### schematic & WAVEFORM

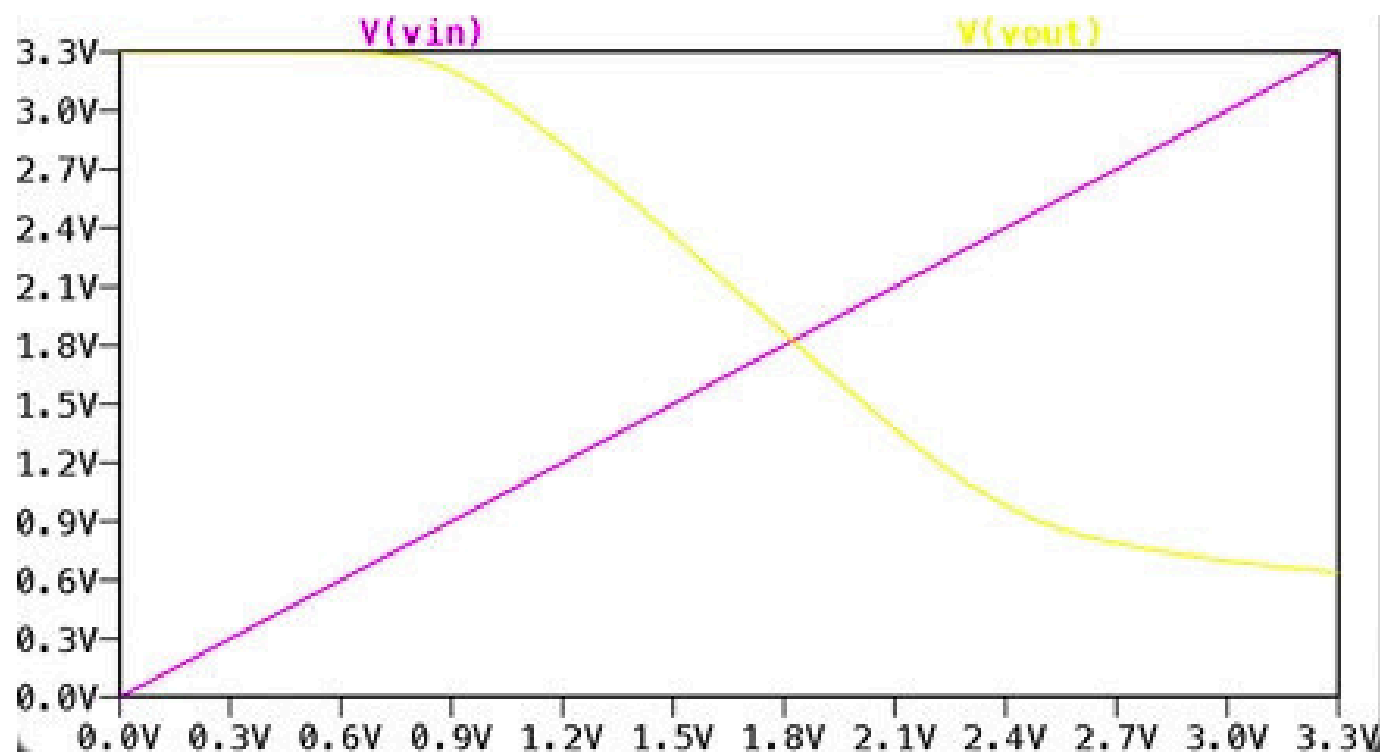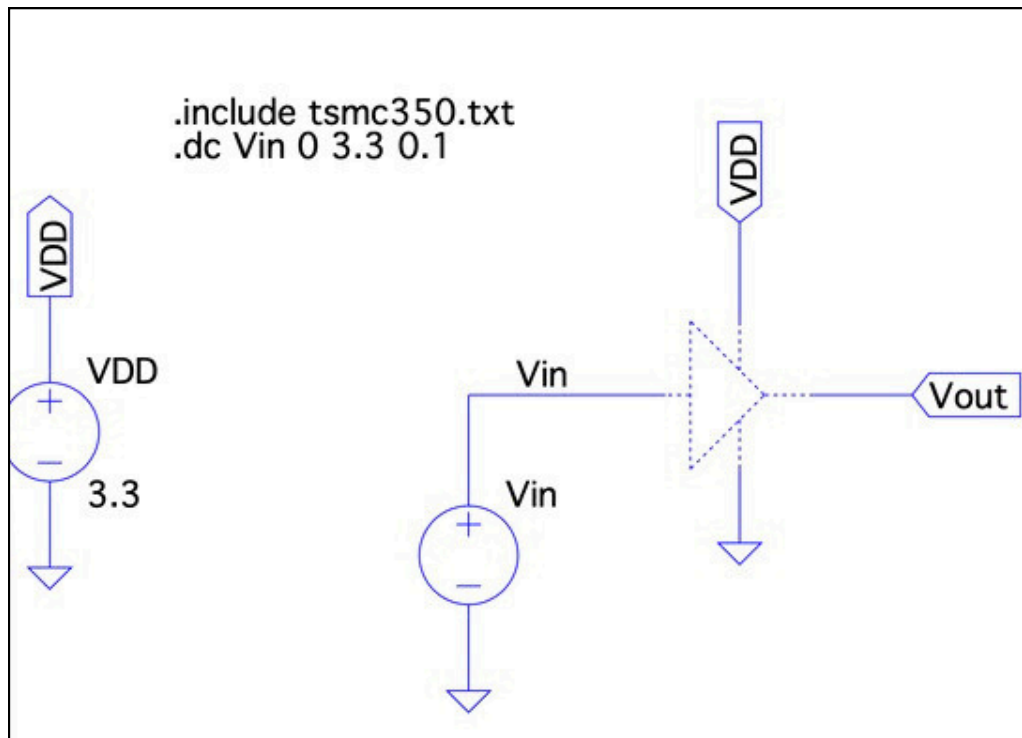


#### observations:

The DC sweep analysis shows that the output voltage decreases as the input voltage increases, confirming the inverting behavior of the common-source NMOS amplifier.

task 5 :

schematic

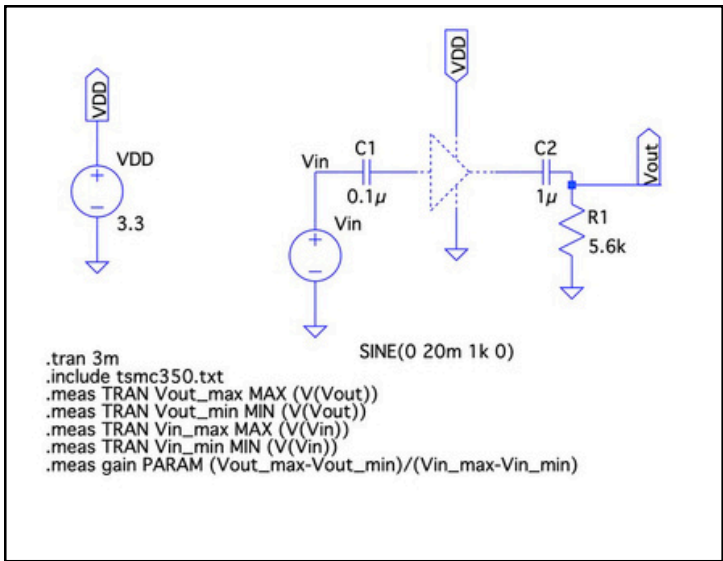

SPICE Output Log

```
lab5task5.log
Search


vout_max: MAX(v(vout))=0.0234521 FROM 0 TO 0.003
vout_min: MIN(v(vout))=-0.022084 FROM 0 TO 0.003
vin_max: MAX(v(vin))=0.0199812 FROM 0 TO 0.003
vin_min: MIN(v(vin))=-0.0199804 FROM 0 TO 0.003
gain: (vout_max-vout_min)/(vin_max-vin_min)=1.13949

Total elapsed time: 0.067 seconds.
```

observations:


AC transient simulation was performed using a small sine input. The output waveform shows clear amplification. The gain was measured successfully using the .meas command GAIN=1.13

WAVEFORM

 

## task 6 :


### schematic

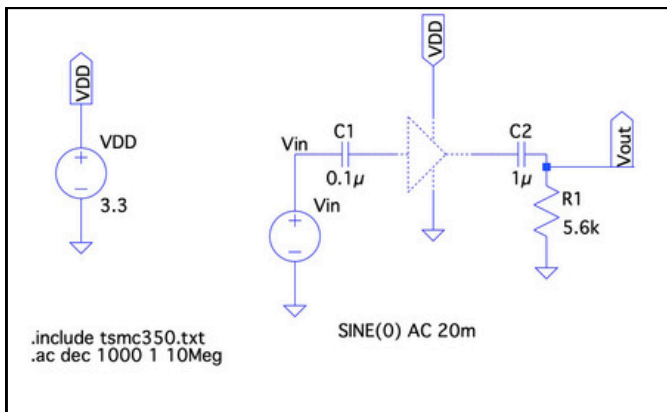

### observations:

The AC sweep analysis shows a low-pass frequency response. The cutoff frequency was identified from the Bode plot  $F_c=30\text{Hz}$

### WAVEFORM

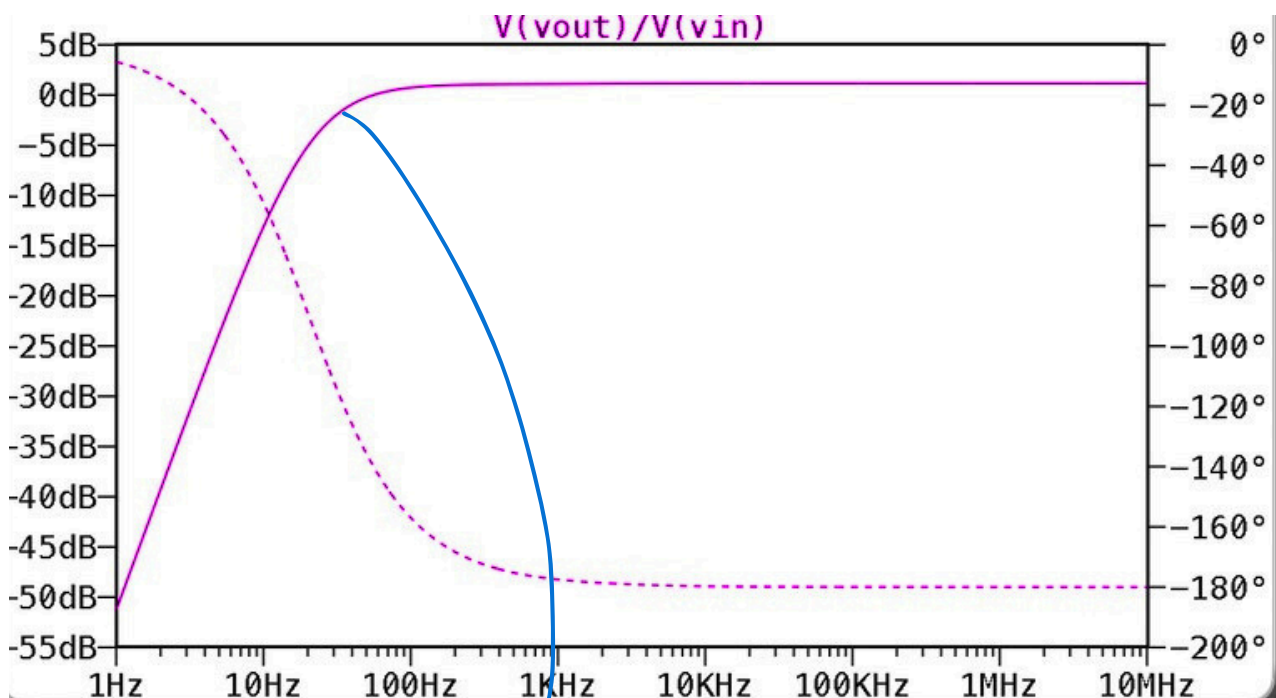

x = 29.620Hz y = -2.053dB, -23.510°